

Basic Electric Circuit Laws

Written by : Antonius Ringlayer (@ringlayer)

<https://ringlayer.wordpress.com> – <http://www.ringlayer.com>- <https://ringlayer.github.io>

There are several electric circuit laws, some famous laws are kirchoff's law and ohm's law.

OHM LAW

Ohm law calculation is the easiest calculation on electric circuits. Ohm law applied in hydraulic mechanism, electric circuits, etc. Ohm's law on electric circuit defines that the pressure (voltage) is the volume of electricity multiplied with the resistance :

$$\mathbf{V = I.R}$$


V = volt , volt is the pressure of electricity.

I = ampere, ampere is volume of electricity

R = resistance

$$\mathbf{I = V/R}$$

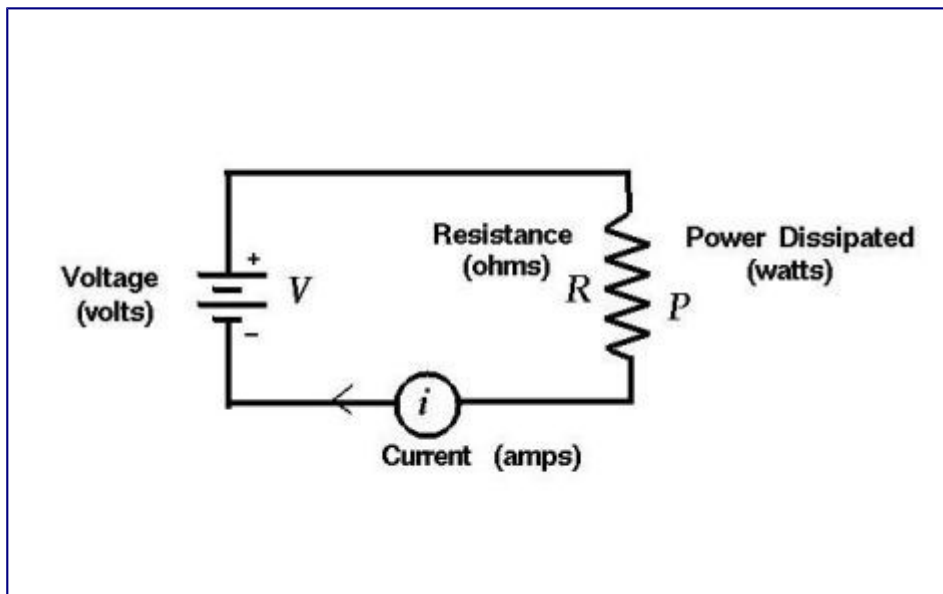as an example we have some little electric circuit :



As an example pressure = 9V, resistance = 220 Ω , So current can be calculated so easily :

$$\mathbf{I = 9/220}$$

So current is:


$$\mathbf{I = 0,04 \text{ ampere}}$$

KIRCHOFF LAW

Kirchoff law defines on the voltage and ampere. Kirchoff's law on current (volume of electricity):

$$\Sigma i = 0$$

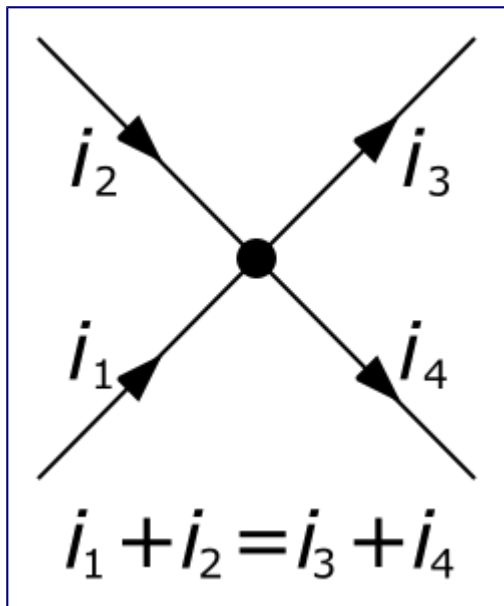As an example here we have simple circuit:



Suppose we will calculate I_4 if:

$I_1 = 0,4 \text{ A}$ (positive current)

$I_2 = 2 \text{ A}$ (positive current)

$I_3 = 1 \text{ A}$ (negative current)

This is the simple algebra:

$$\Sigma i = 0$$

$$i_1 + i_2 = i_3 - i_4$$

$$i_1 + i_2 - i_3 - i_4 = 0$$


$$(0,4 + 2) - 1 - i_4 = 0$$

$$i_4 = 2,4 - 1 = \mathbf{1,4 \text{ A}}$$

Second law is kirchoff pressure law:

$$\Sigma v = 0$$

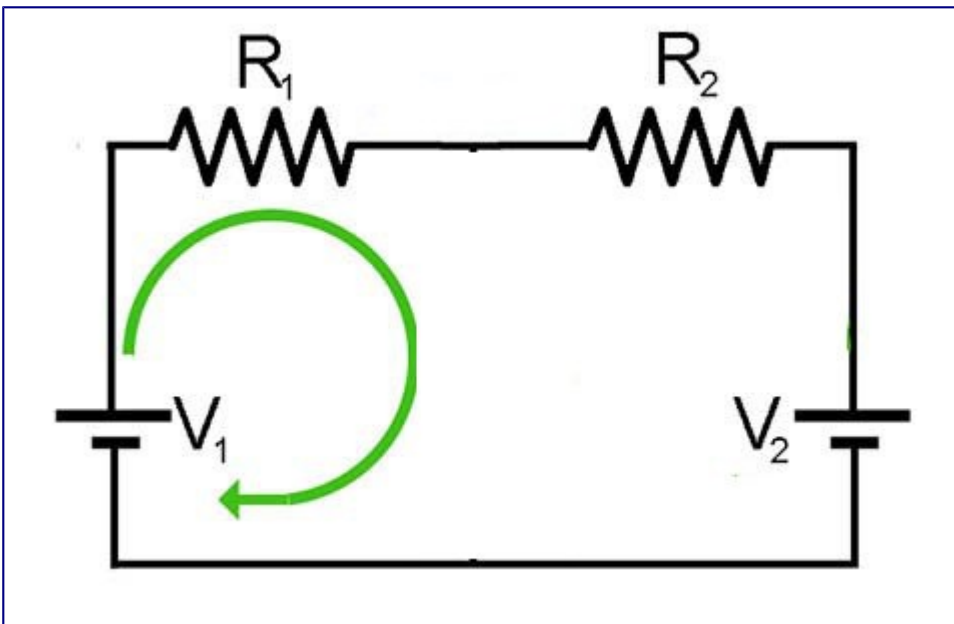For an example we have a simple electric circuit:



Suppose:

$$v_1 = 20 \text{ volt}$$

$$v_2 = 10 \text{ volt}$$

$$R_1 = 110 \, \Omega$$

$$R_2 = 220 \, \Omega$$

Current (I) calculation is simple :

Since $\sum v = 0$:

$$V_1 - (I * R_1) - V_2 - (I * R_2) = 0$$

$$20 - (I * 110) - 10 - (I * 220) = 0$$

$$10 - (I * 110) - (I * 220) = 0$$

$$10 = (I * 110) + (I * 220)$$

$$10 = i * 330$$

$$I = 10/330$$

$$\mathbf{I = 0.030}$$

So the current is 0,030 ampere.