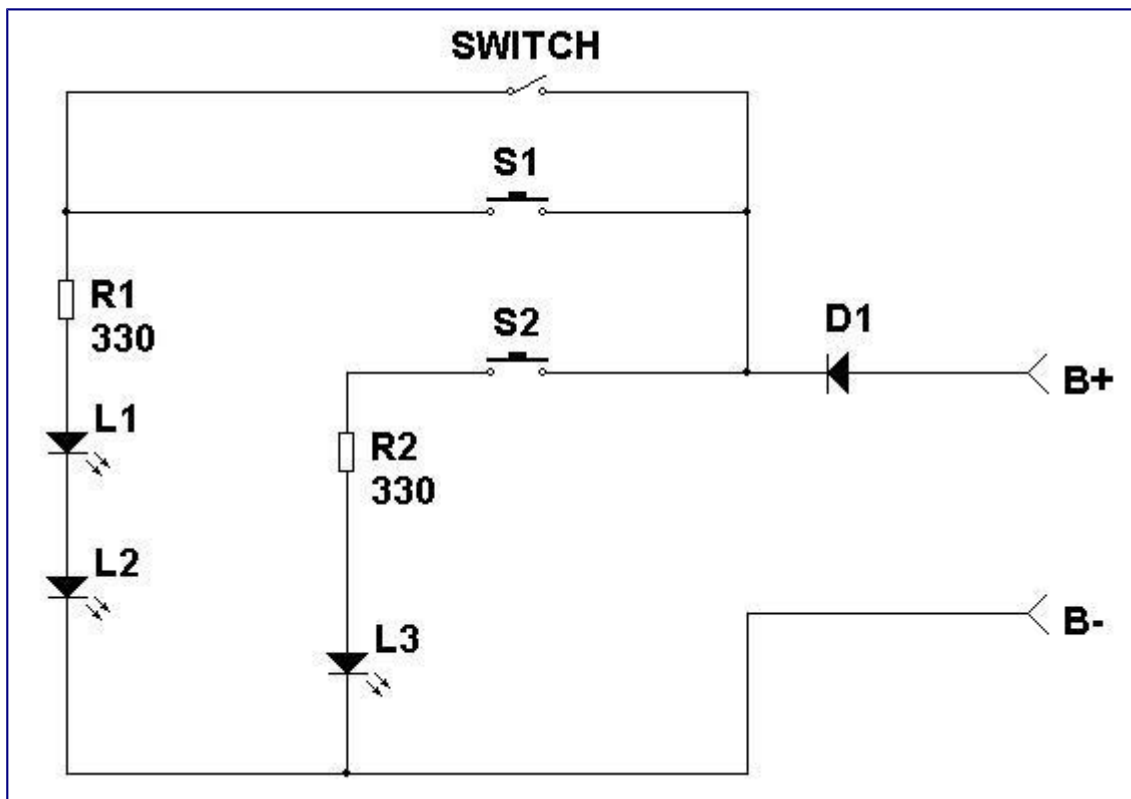


Making an Electronic Torch – Schematic, PCB Version and Breadboard Version

Written by : Antonius Ringlayer (@ringlayer)

<https://ringlayer.wordpress.com> – <http://www.ringlayer.com> - <https://ringlayer.github.io>

Electronic Torch is an unique electronic circuit to learn about how electric flow through each components. Below is the electronic circuit:



Part Lists Based on Above Schematic

- 2 resistor 330 ohm or 320 ohm. (breadboard version can uses up to 3 resistors)
- 3 led
- 3 switch
- 1 Dioda in4001

How this works on PCB Version ?

Below is the electronic circuit logic flow :

– If switch is on, the current will flow through:

D1 (since it's a dioda it will prevent reverse current) -> switch -> R1 -> led1 -> led2 -> ground


– If s1 is on, the current will flow through:

D1 -> S1 -> R1 -> led1 -> led2 -> ground.

– if s2 is on, the current will flow through:

D1 -> S2 -> R2 -> led 3 -> ground

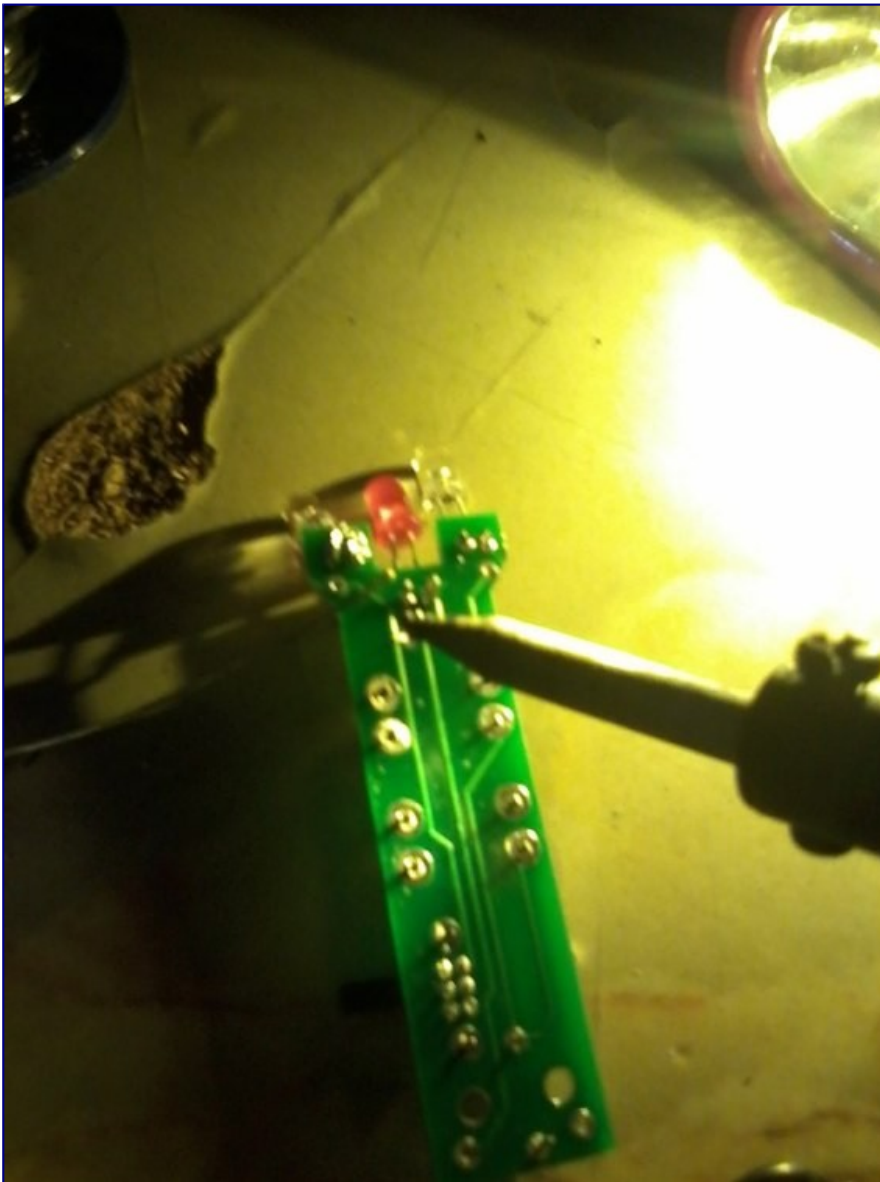Solder each component based on above schematic




Note:

– Clean your solder with sponge before soldering

- Before soldering drop some soldering tin on top of your solder
- Don't use too much soldering tin

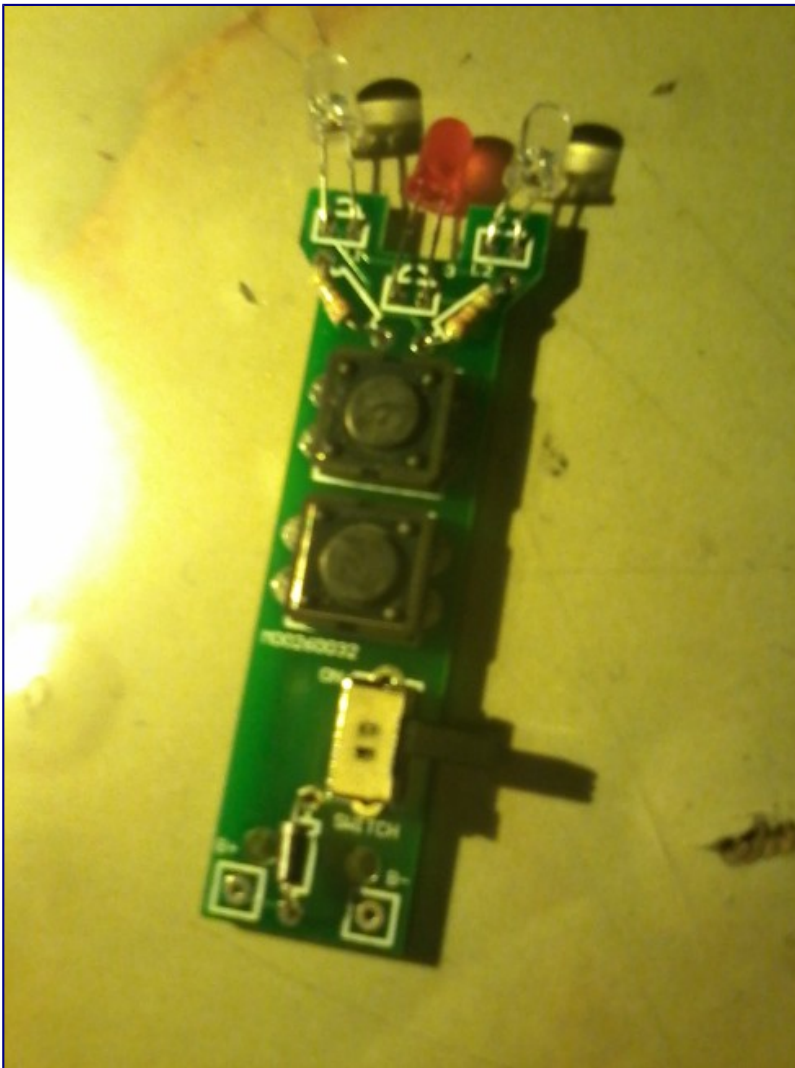And here comes the pcb version of the torch :



Breadboard Version

We can also making breadboard version, vero board version, and so on. Here's the breadboard version of this electronic torch with 3 resistor (1 resistor 330 ohm and 2 resistor 320 ohm).

